



الامتحان مكون من أربع صفحات، الإجابة في نفس ورقة الأسئلة، النهاية العظمى 100 درجة.
الإجابة النهائية يجب أن تكون مكتوبة في المكان المخصص لها وخطوات الحل تكون في الصفحة المقابلة.

Attempt all questions, full mark: 100 Points

Time: 3 Hours

Question #1: (8 Points)

Design a difference amplifier (Fig.1) to meet the following criteria: $V_{out} = 3V_b - 4V_a$. The resistance seen by the signal source V_a is 22 k Ω when V_b is zero, and the resistance seen by the signal source V_b is 500 k Ω .

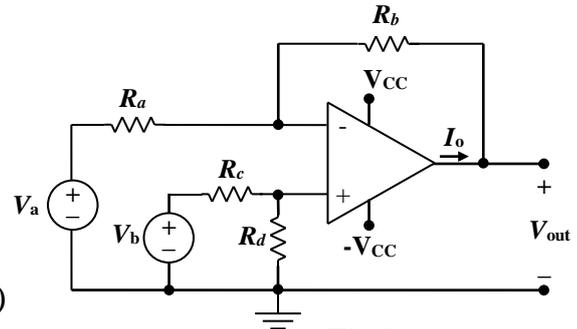


Fig.1

- a) Specify the values of R_a , R_b , R_c , and R_d . (6 Points)
b) If $V_a = 1.25$ V and $V_b = 4$ V, find I_o . (2 Points)

a) $R_a = 22 \text{ K}\Omega$

$R_b = 88 \text{ K}\Omega$

$R_c = 200 \text{ K}\Omega$

$R_d = 300 \text{ K}\Omega$

b) $I_o = 0.052 \text{ mA}$

Question #2: (20 Points)

The switch in the circuit of Fig.2 have been in position (a) for a long time. At $t = 0$, the switch moves to position (b). The switch remains in position (b) a time equals t_1 until the voltage v becomes 5 V, then it moves again to position (a).

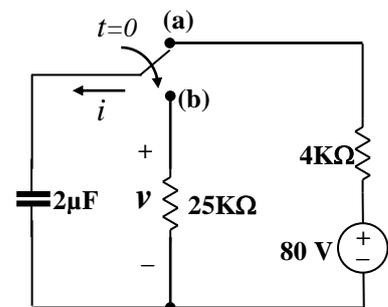


Fig. 2

- a) Find $v(t)$ for $0 \leq t \leq t_1$. (8 Points)
b) Find the time t_1 . (4 Points)
c) Find the current $i(t)$ for $t_1 \leq t \leq \infty$. (8 Points)

a) $v(0^+) = 80 \text{ V}$

$v(\infty) = 0$

$\tau_1 = 50 \text{ mS}$

$v(t) = 80 e^{-t/50}$, (t in mSec)

b) $t_1 = 138.6 \text{ mS}$

c) $i(t_1) = 18.75 \text{ mA}$

$i(\infty) = 0$

$\tau_2 = 8 \text{ mS}$

$i(t) = 18.75 e^{-(t-138.6)/8}$

Question #3: (14 Points)

The two switches in the circuit of Fig.3 operate synchronously. Switch (1) has been in position (a) and switch (2) is closed for a long time, at $t= 0$, switch (1) moves instantaneously to position (b) and switch (2) is open. Find $v_c(0^+)$, $v_c(\infty)$, $i_L(0^+)$, $[dv_c/dt]_{0^+}$, the roots of the characteristic equation s_1 , s_2 and $v_c(t)$ for $t \geq 0$.

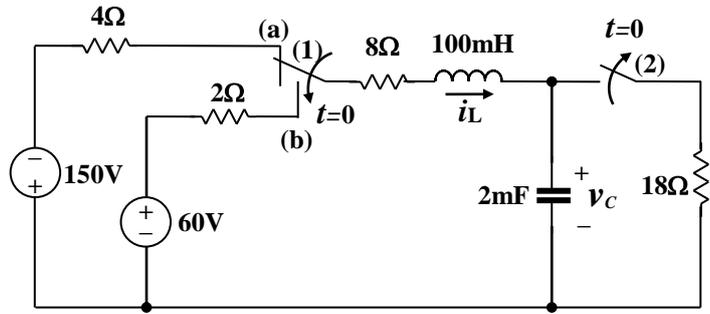


Fig. 3

$v_c(0^+) = -90 \text{ V}$

$v_c(\infty) = 60 \text{ V}$

$i_L(0^+) = -5 \text{ A}$

$[dv_c/dt]_{0^+} = -2500 \text{ V/Sec}$

$s_1 = -50 + j50$

$s_2 = -50 - j50$

$v_c(t) = 60 - e^{-50t} (150 \cos 50t + 200 \sin 50t) \text{ volts}$

Question #4: (12 Points)

3. A balanced Δ -connected load has an impedance of $180 + j75 \Omega/\phi$. The load is fed through lines having an impedance of $1 + j1 \Omega/\text{line}$. The phase voltage at the terminals of the load is 1950V. Calculate:
- The magnitude of the phase current at the load.
 - The magnitude of the line current.
 - The magnitude of the line voltage at the sending end.
 - The total power dissipated in the load.

The magnitude of the phase current at the load **10 A**

The magnitude of the line current..... **17.3 A**

The magnitude of the line voltage at the sending end **1989.3 V**

The total power dissipated in the load..... **54 KW**

Question #5: (12 Points)

The two switches in the circuit shown in Fig.5 operate simultaneously. There is no energy stored in the circuit at the instant the switches close. Find the s-domain Thevenin equivalent of the circuit to the left of the terminals (a), (b), then find $I(s)$ and $i(t)$ for $t \geq 0$.

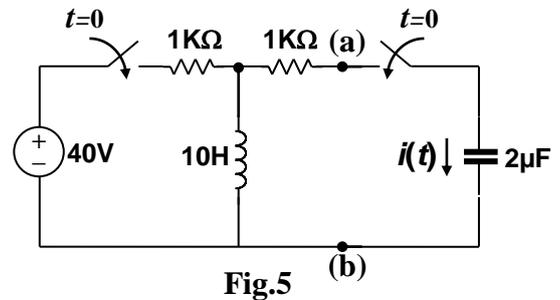


Fig.5

$$V_{Th}(s) = \frac{40}{s+100} \text{ V. Sec}$$

$$Z_{Th}(s) = 2000 \frac{s+50}{s+100} \Omega$$

$$I(s) = \frac{s/50}{s^2+300s+25 \times 10^3}$$

$$i(t) = 0.0632 e^{-150t} \cos(50t + 71.6^\circ) \text{ A}$$

Question #6: (12 Points)

Find the current I_1 , I_2 and the voltage V_o in the circuit of Fig.6

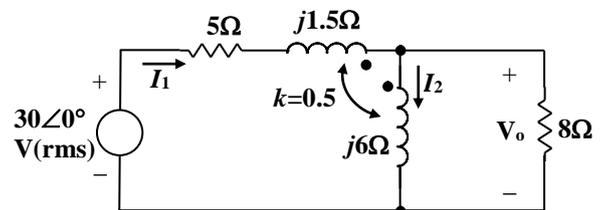


Fig.6

The first loop equation

$$5 I_1 + j4.5 I_2 = 30$$

The second loop equation

$$-(8 + j1.5)I_1 + (8 + j6)I_2 = 0$$

$$I_1 = 4.06 \angle -26.39^\circ \text{ A} = 3.64 - j1.8 \text{ A}$$

$$I_2 = 3.3 \angle -52.64^\circ \text{ A} = 2 - j0.82 \text{ A}$$

$$V_o = 14.66 \angle 26.6^\circ \text{ V} = 13.12 + j6.56 \text{ V}$$

Question #7: (14 Points)

The Fourier series of the half-wave rectified sinusoidal voltage:

$$v(t) = V_M \sin(\omega_o t), \quad 0 \leq t \leq \frac{T}{2};$$


$$v(t) = 0, \quad \frac{T}{2} \leq t \leq T$$

is given by:

$$v(t) = \frac{V_M}{\pi} + \frac{V_M}{2} \sin(\omega_o t) - \frac{2V_M}{\pi} \sum_{n=1}^{\infty} \frac{\cos(2n\omega_o t)}{4n^2 - 1}.$$

A half-wave rectified sinusoidal voltage having $V_M = 100 \text{ V}$ and $\omega_o = 800 \text{ rad/s}$ is applied to the circuit of Fig.7. Find:

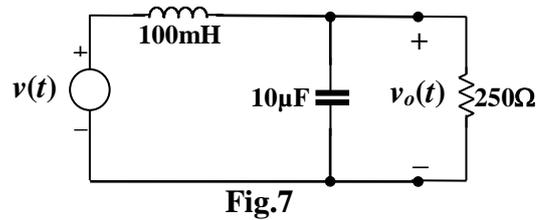- a) The magnitude of the first three non-zero terms of the output voltage. (6 Points)
- b) The RMS value of the input voltage. (4 Points)
- c) The RMS value of the output voltage. (4 Points)



$V_{o(dc)} = 100/\pi \text{ V}$	$V_{o(1)} = 103.8 \text{ V}$	$V_{o(2)} = 12.6 \text{ V}$
$V_{in(RMS)} = 50 \text{ V}$		$V_{o(RMS)} = 80.5 \text{ V}$

Question #8: (8 Points)

The following dc measurements were made on the resistive network shown in Fig.8


Measurement 1:

$$V_1 = 4\text{V}, I_1 = 44 \text{ mA}, V_2 = 0, I_2 = -200 \text{ mA}$$

Measurement 2:

$$V_1 = 20 \text{ V}, I_1 = 20 \text{ mA}, V_2 = 4 \text{ V}, I_2 = 0$$

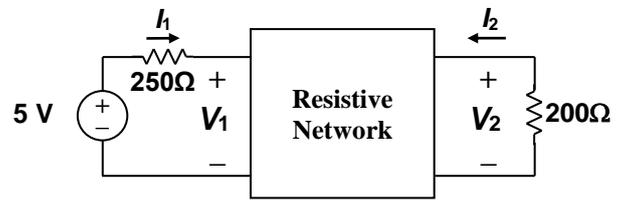- a) Find the transmission (*a*) parameters of the circuit. (4 Points)
- b) Find $V_1, V_2, I_1,$ and I_2 . (4 Points)



$a_{11} = 5$	$a_{12} = 20 \Omega$	$a_{21} = 5 \text{ mS}$	$a_{22} = 0.22$
$V_1 = 3.85 \text{ V}$	$V_2 = 0.754 \text{ V}$	$I_1 = 4.6 \text{ mA}$	$I_2 = -3.77 \text{ mA}$